



# EXPERIMENT - 1

Switching Theory and Logic Design (STLD)

## Aim

Realize all gates by verifying their truth tables.

Syeda Reeha Quasar  
14114802719  
3C7

## EXPERIMENT – 1

**AIM:** Realize all gates by verifying their truth tables.

**HARDWARE REQUIRED:** Power supply/ Voltage supply, Bread Board, Resistors, LEDs, Connecting Wires, Integrated Chips ICs (7404, 7408, 7432, 7486, 7400, 7402, 74266)

**SOFTWARE REQUIRED:**


Software stimulator (MULTISIM) - [www.multisim.com](http://www.multisim.com) (free software)

Stimulating schematic models of desired circuits


Components used - Source (Clock Voltage), Passive elements (resistor), Digital components (AND, OR, NAND, NOR, XOR, XNOR, Inverter), Probe for Analysis and annotation (Digital), Schematic connectors (Ground)

**CIRCUIT:**


AND GATE

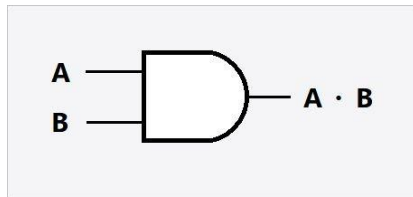


OR GATE

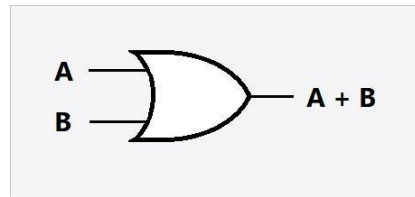


NAND GATE


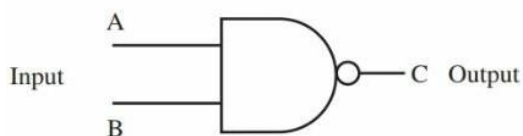


NOR GATE

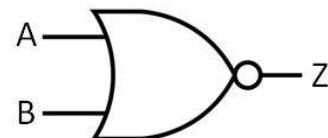


NOT GATE

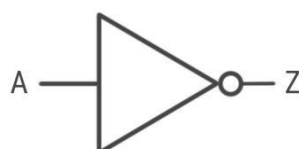

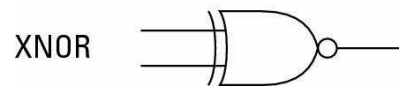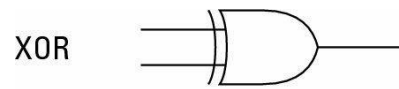


## PIN - DIAGRAM:


### AND GATE

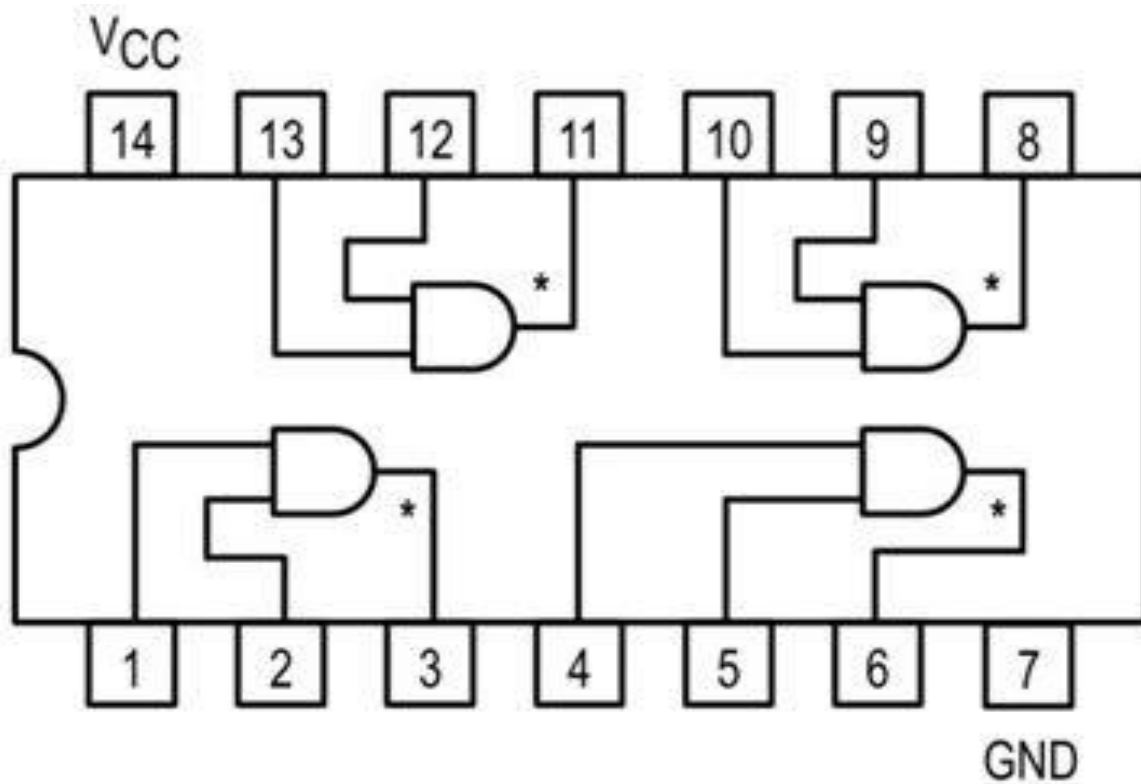


### NAND GATE

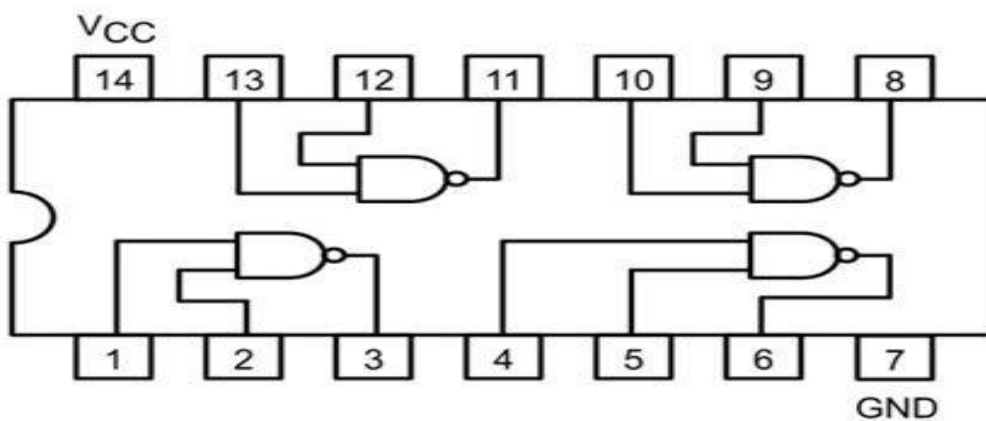


## OR GATE

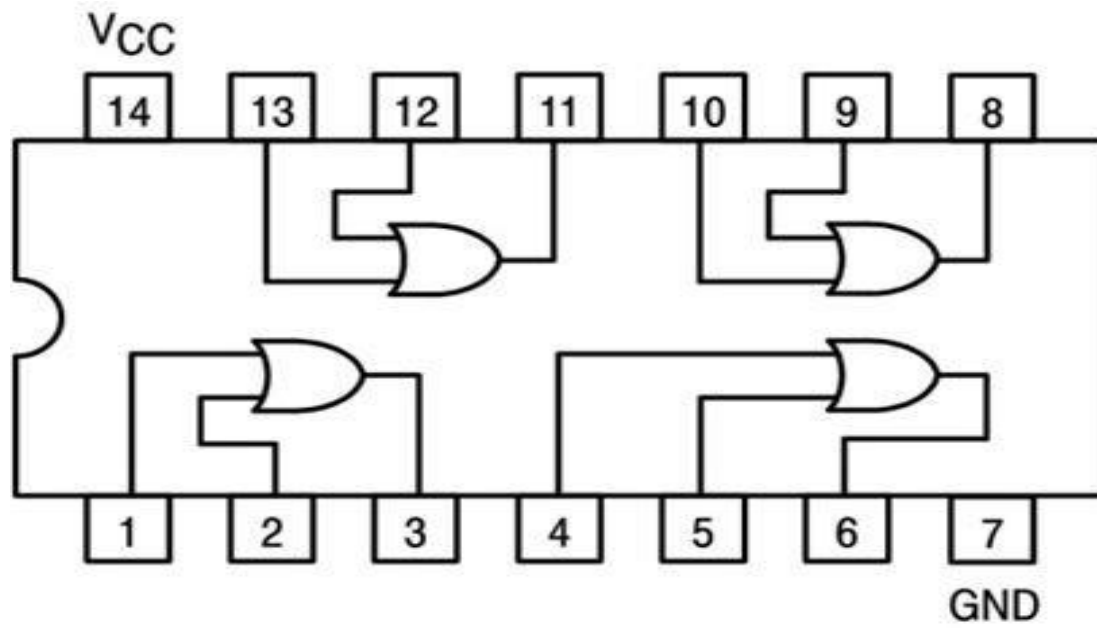


## NOR GATE

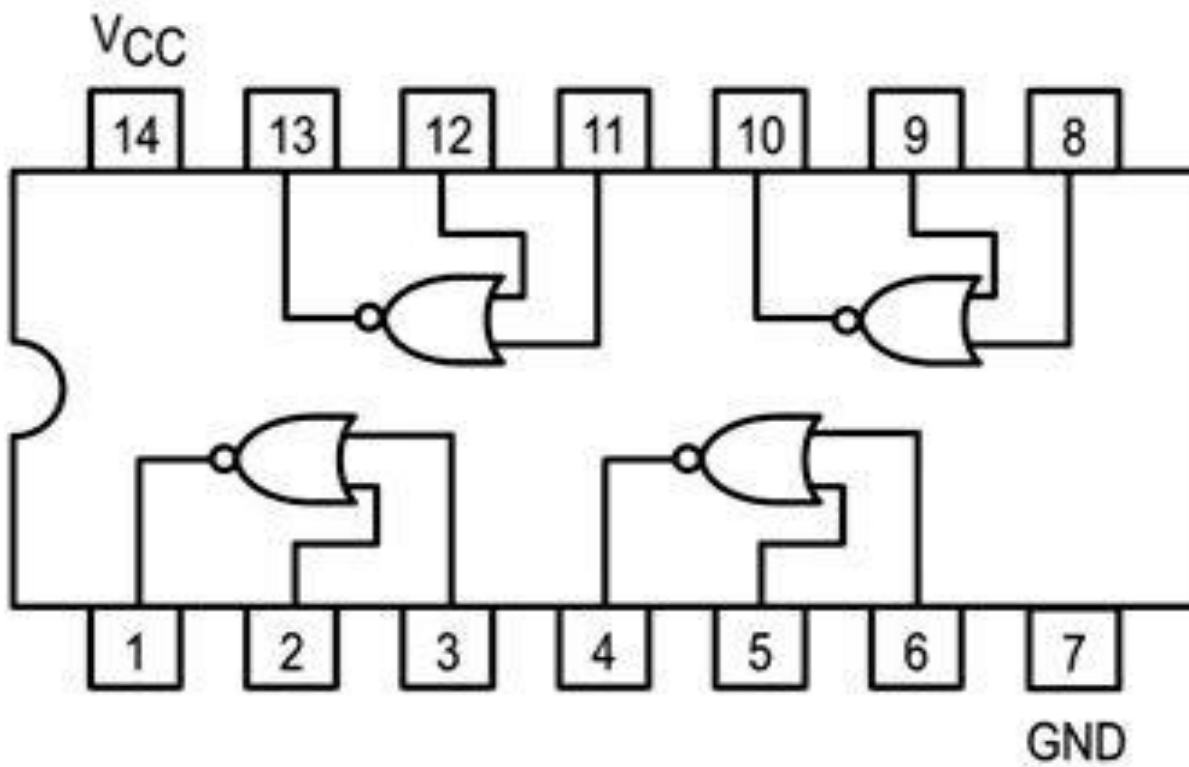


## XOR GATE

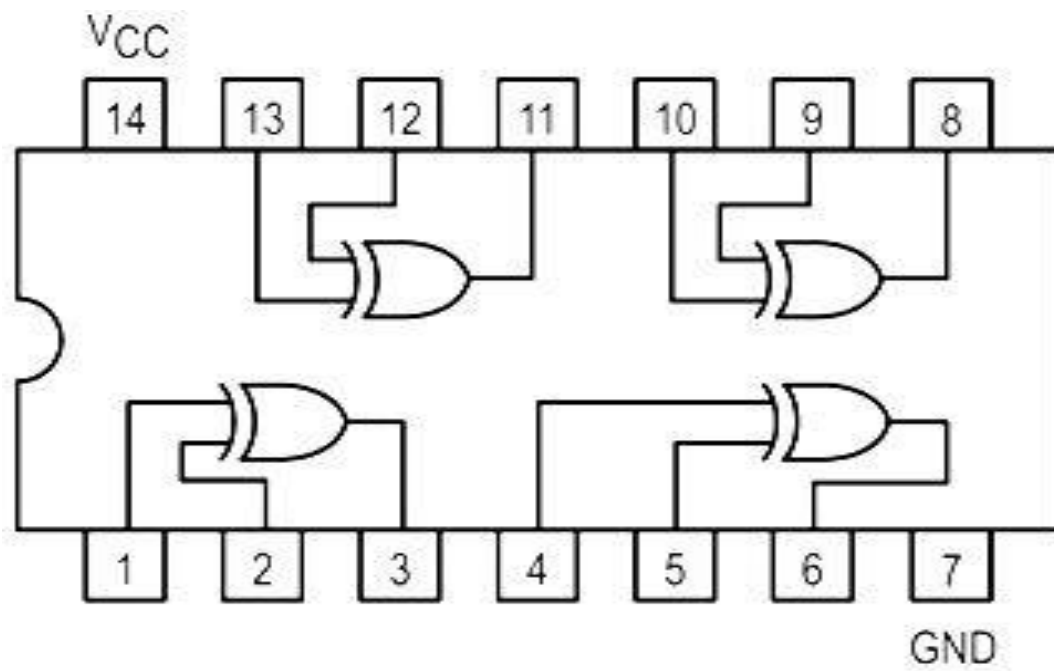

## XNOR GATE

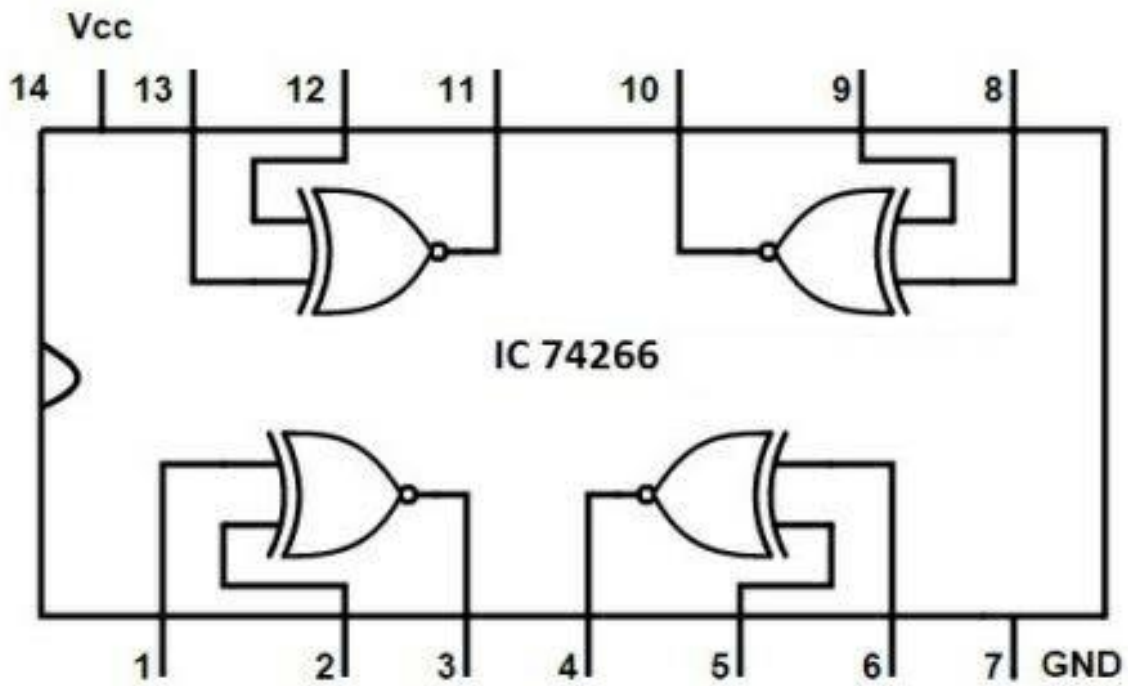

## NOT GATE

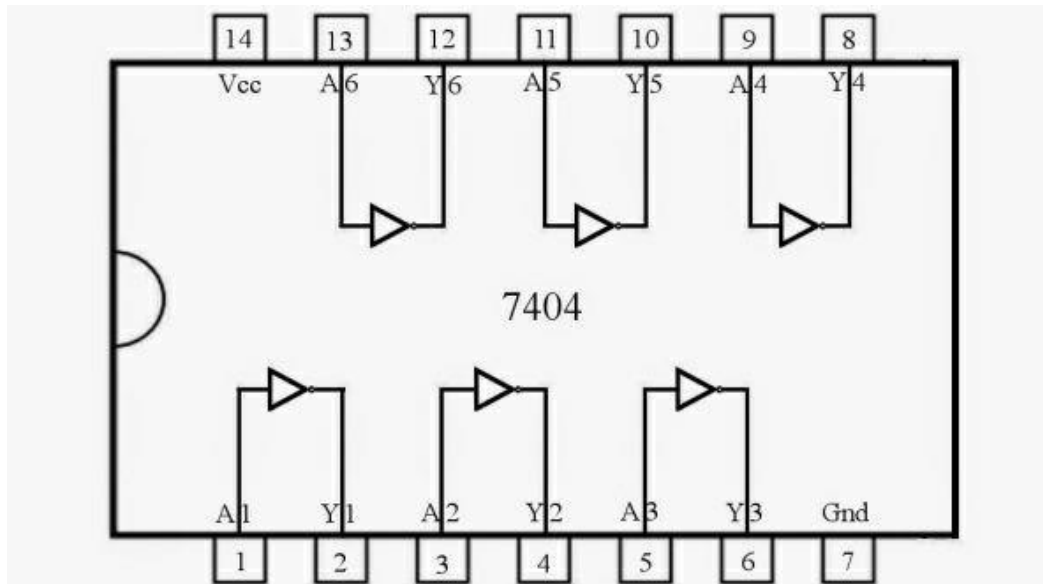

## TRUTH TABLES

AND Truth Table		
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

NAND Truth Table		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

NOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

NOT Truth Table	
A	Q
0	1
1	0

XOR Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Or Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

**THEORY:** Logic gates are electronic circuits which perform logical operations on one or more inputs to produce a signal output. There are 7 logic gates. These include the AND, NAND, OR, NOR, XOR, XNOR and NOT.

#### PROCEDURE (MULTISIM):

- Make the circuits shown as shown in the figures.
- Select the required components (gates, resistor, voltage sources (Clock Voltage) and ground symbols from the tool bar on the left.
- Ground both the voltage sources (clock Voltages) and then connect them to the input terminal of the gate.
- Connect the output terminal to 1 k ohm resistor and ground it.

#### Precautions:

- Power supply should not exceed 5V.
- All the connections should be tight.
- Components should be tested before the practical.

## NOT GATE

OPEN CIRCUIT

DELETE

EDIT DETAILS

< > ^ v 🔍

MULTISIM SHARE

SOCIAL SHARE

CIRCUIT DESCRIPTION

CREATOR

reeha  
7 Circuits

DATE CREATED  
0 minutes ago

LAST MODIFIED  
0 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)

MOST POPULAR CIRCUITS

Online simulator  
by Electrolforno

99606 ★ 11 339

Simple Buck Converter  
by OStep

35348 ★ 22 268

< > ^ v 🔍

DATE CREATED  
0 minutes ago

LAST MODIFIED  
0 minutes ago

[EDIT TAGS](#)

MULTISIM SHARE

CIRCUIT DESCRIPTION

No description has been provided for this circuit. [EDIT DESCRIPTION](#)

Digital

Time (s)

62m 62.5m 63m 63.5m 64m 64.5m 65m 65.5m 66m 66.5m

PR1: D(2)

PR2: D(1)

Digital to Analog Converter - DAC  
by SILRing

24061 ★ 31 98



## XNOR GATE

MultisimLive


FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

XNOR Gate

★ Favorite 0 Copy 0 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

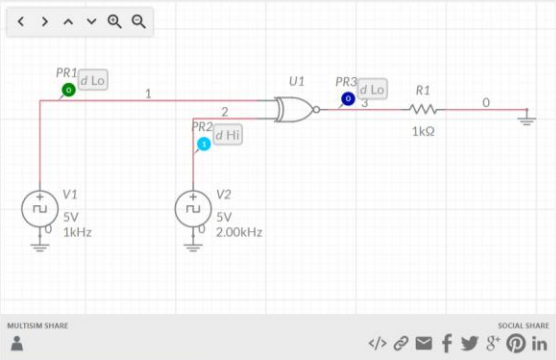

CREATOR

reeha 7 Circuits

DATE CREATED 2 minutes ago LAST MODIFIED 2 minutes ago

TAGS

This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

Online simulator by Electronferno

99606 ★ 11 339

Simple Buck Converter by OStep

268

MULTISIM SHARE

SOCIAL SHARE

Waiting for faye.getstream.io...

Type here to search

13:34 26-08-2020


MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

Circuit Graph

Interactive 1

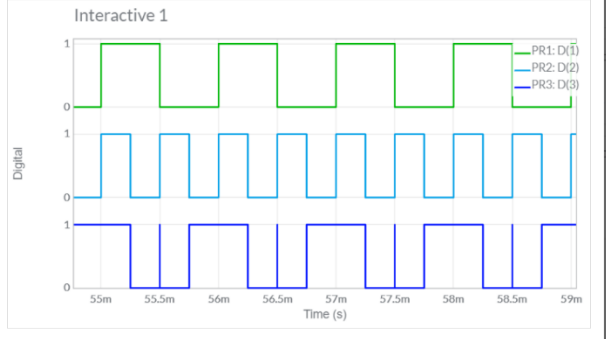

Comments (0)

There are currently no comments

Waiting for faye.getstream.io...

Type here to search

13:34 26-08-2020

# XOR GATE

MultisimLive


FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

OPEN CIRCUIT

DELETE EDIT DETAILS

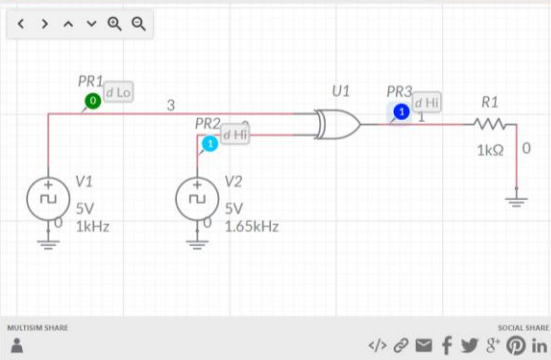

CREATOR

reeha  
7 Circuits

DATE CREATED  
5 minutes ago

LAST MODIFIED  
5 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)

MOST POPULAR CIRCUITS

Online simulator  
by Electronferno

99606 11 339

Simple Buck Converter  
by OStep

35348 22 268

CIRCUIT DESCRIPTION

Waiting for faye.getstream.io...

Type here to search

MultisimLive


FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

OPEN CIRCUIT

DELETE EDIT DETAILS

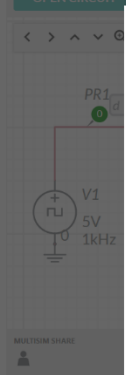

CREATOR

reeha  
7 Circuits

DATE CREATED  
5 minutes ago

LAST MODIFIED  
5 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)

MOST POPULAR CIRCUITS

Online simulator  
by Electronferno

99606 11 339

Simple Buck Converter  
by OStep

35348 22 268

Digital to Analog Converter - DAC  
by SILRing

CIRCUIT DESCRIPTION


No description has been provided for this circuit. [EDIT DESCRIPTION](#)

Waiting for faye.getstream.io...

Type here to search

Circuit Graph

Interactive 1

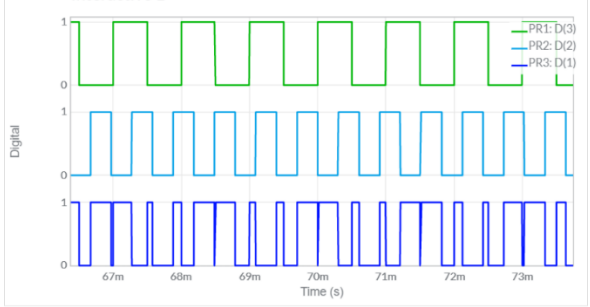

## NOR GATE


MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

### NOR Gate

OPEN CIRCUIT DELETE EDIT DETAILS

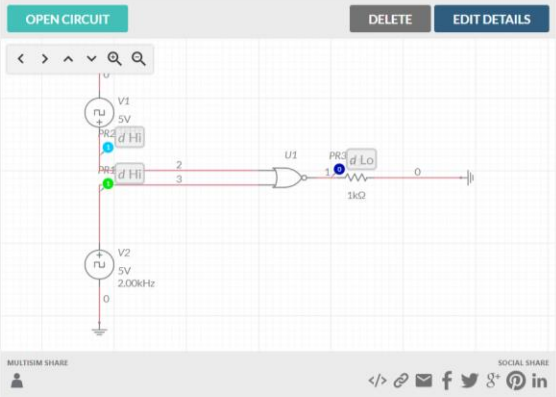

CREATOR: reeha, 7 Circuits

DATE CREATED: 15 minutes ago LAST MODIFIED: 8 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno (99606 views, 11 stars, 339 downloads)
- Simple Buck Converter by OStep (35348 views, 22 stars, 268 downloads)

CIRCUIT DESCRIPTION

Windows taskbar: Type here to search, 13:34, 26-08-2020


MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

### Circuit Graph

Interactive 1



Legend: PR1: D(3), PR2: D(2), PR3: D(1)

Time (s): 217.5m, 218m, 218.5m, 219m, 219.5m, 220m

CIRCUIT GRAPH

Windows taskbar: Type here to search, 13:35, 26-08-2020

## OR GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

### OR Gate

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 7 Circuits

DATE CREATED: 11 minutes ago

LAST MODIFIED: 11 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

CIRCUIT COPIED FROM: NOR Gate

MOST POPULAR CIRCUITS

- Online simulator by Electronforno 99606 11 339
- Simple Buck Converter

MULTISIM SHARE

CIRCUIT DESCRIPTION

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

### Circuit Graph

Interactive 1

PR1: D(1)  
PR2: D(2)  
PR3: D(3)

Time (s)

There are currently no comments

# NAND GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

NAND Gate

Favorite 0 Copy 0 Views 1

OPEN CIRCUIT

DELETE

EDIT DETAILS

< > ^ v 🔍

MULTISIM SHARE

</> 📧 📱 📺

CREATOR

reeha  
7 Circuits

DATE CREATED  
14 minutes ago

LAST MODIFIED  
14 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)

MOST POPULAR CIRCUITS

Online simulator  
by ElectroInferno

99606 ★ 11 339

Simple Buck Converter  
by Ostep

268 38

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

Circuit Graph

×

Interactive 1

PR1: D(1)

PR2: D(2)

PR3: D(3)

Comments (0)

There are currently no comments

## AND GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 7 Circuits

DATE CREATED: 33 minutes ago LAST MODIFIED: 27 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS



MOST POPULAR CIRCUITS

- Online simulator by Electronforno 99606 stars 11 339
- Simple Buck Converter by OStep 35348 stars 22 268

CIRCUIT DESCRIPTION

Waiting for faye.getstream.io...

Type here to search

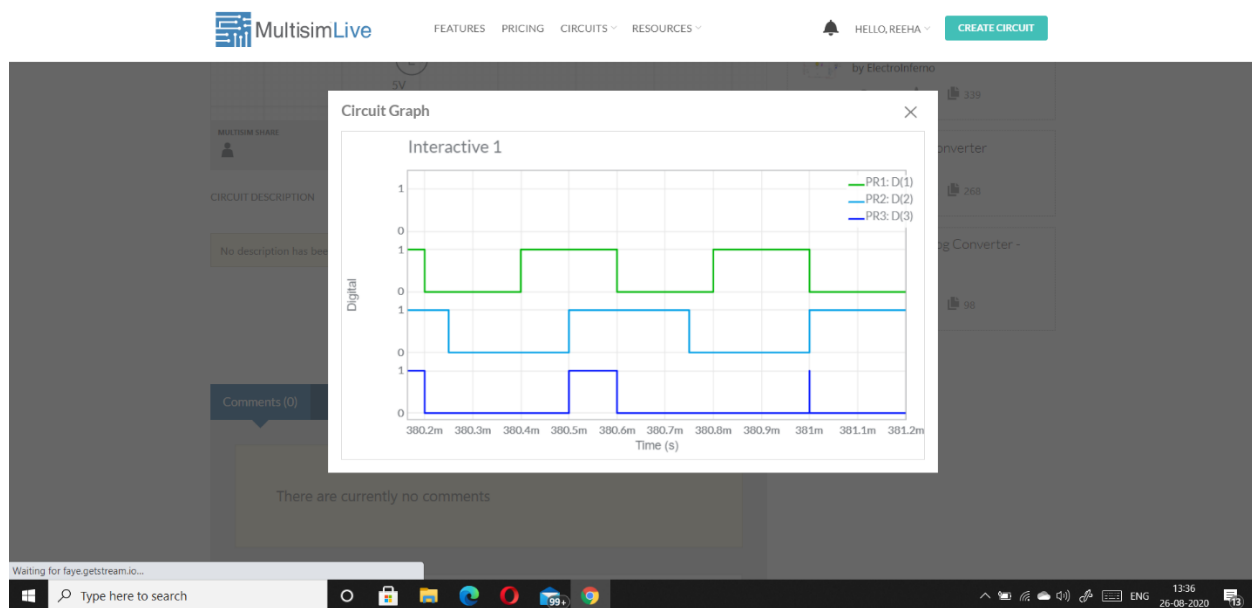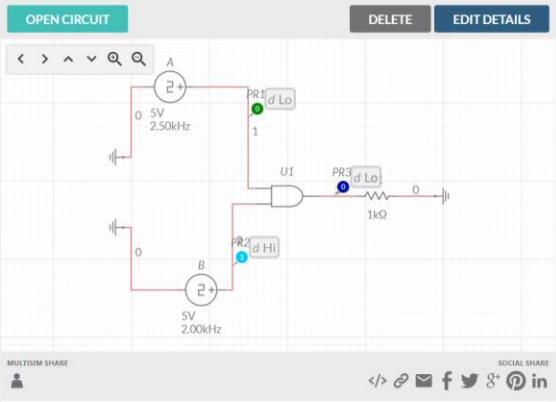

**Result:**

**All Gates has been realized.**

## VIVA VOCE

**Q1. Explain what is Boolean Algebra?**

Boolean algebra is a mathematic system of logic in which truth functions are expressed as symbols and then these symbols are manipulated to arrive at conclusion.

**Q2. Explain what are the basic logic elements?**

Basic logic elements are NOT gate, AND gate, OR gate and the flip-flop.

**Q3. Explain what is a truth table?**

Truth table is a table that gives outputs for all possible combinations of inputs to a logic circuit.

**Q4. Define positive logic and negative logic.**

If the higher of the two voltages represents a 1 and the lower voltage represents a 0, then the logic is called a positive logic. On the other hand, if the lower voltage represents a 1 and the higher voltage a 0, we have a negative logic.

**Q5. Explain what is pulse logic system?**

A logic system in which a bit is recognized by the presence or absence of a pulse is called a pulse or dynamic logic system.