



EXPERIMENT - 9

Switching Theory and Logic Design (STLD)

Aim

To realize 4-Bit Binary to BCD Converter.

Syeda Reeha Quasar
14114802719
3C7

EXPERIMENT - 9

AIM:

To realize 4-Bit Binary to BCD Converter.

Hardware and Software Apparatus Required

Hardware:

Breadboard, IC 7400 (NAND), IC 7410 (3 input NAND), IC 7404 (NOT), LEDs, 5V power supply, connecting wires.

Software Simulation:

The schematic models of the desired circuits will be stimulated on MULTISIM (Free Software), easily accessible at www.multisim.com.

Components used – Source (Clock Voltage), Passive elements (resistor), Digital components (AND, OR, NAND, NOR, XOR, XNOR, Inverter), Probe for Analysis and annotation (Digital), Schematic connectors (Ground)

Theory:

BCD is binary coded decimal number, where each digit of a decimal number is respected by its equivalent binary number. That means, LSB of a decimal number is represented by its equivalent binary number and similarly other higher significant bits of decimal number are also represented by their equivalent binary numbers.

For example, BCD Code of 14 is-



Let us design a 4 bit **binary to BCD code converter**. As the 4 bit can

represent 0 to 15, we can draw the conversion table as follows,

Binary Code	Decimal Number	BCD Code
A B C D		B ₅ B ₄ B ₃ B ₂ B ₁
0 0 0 0	0	0 0 0 0 0
0 0 0 1	1	0 0 0 0 1
0 0 1 0	2	0 0 0 1 0
0 0 1 1	3	0 0 0 1 1
0 1 0 0	4	0 0 1 0 0
0 1 0 1	5	0 0 1 0 1
0 1 1 0	6	0 0 1 1 0
0 1 1 1	7	0 0 1 1 1
1 0 0 0	8	0 1 0 0 0
1 0 0 1	9	0 1 0 0 1
1 0 1 0	10	1 0 0 0 0
1 0 1 1	11	1 0 0 0 1
1 1 0 0	12	1 0 0 1 0
1 1 0 1	13	1 0 0 1 1
1 1 1 0	14	1 0 1 0 0
1 1 1 1	15	1 0 1 0 1

Here, B₅ bit represents MSB of decimal number and B₄, B₃, B₂, B₁ represents 4 bit binary equivalent of LSB of decimal number.


From, above conversion table, we can write SOP form for different bits of BCD code.

$$B_5 = \sum m(10, 11, 12, 13, 14, 15), \quad B_4 = \sum m(8, 9), \quad B_3 = \sum m(4, 5, 6, 7, 14, 15),$$

$$B_2 = \sum m(2, 3, 6, 7, 12, 13), \quad B_1 = \sum m(1, 3, 5, 7, 9, 11, 13, 15)$$


TRUTH TABLE :

AND




INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

NOT



INPUT	OUTPUT
A	
0	1
1	0

OR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

K - map for B_5

AB \ CD				
	00	01	11	10
00				
01				
11	1	1	1	1
10			1	1

$$B_5 = AB + BC$$

K - map for B_4

AB \ CD				
	00	01	11	10
00				
01				
11				
10	1	1		

$$B_4 = \overline{A}\overline{B}\overline{C}$$

K - map for B_3

AB \ CD				
	00	01	11	10
00				
01	1	1	1	1
11	1	1	1	1
10				

$$B_3 = \overline{A}B + CB$$

K - map for B_2

AB \ CD				
	00	01	11	10
00			1	1
01			1	1
11	1	1		
10				

$$B_2 = ABC + \overline{A}C$$

K - map for B_1

AB \ CD		CD			
		00	01	11	10
AB	00		1	1	
	01		1	1	
	11		1	1	
	10		1	1	

$$B_1 = D$$



Procedure:

1. Check all the components for their working.
2. Insert the appropriate IC into the IC base.
3. Make connections as shown in the circuit diagram.
4. Verify the results and observe the outputs.

Multisim:

1. Click on the 'Create Circuit' option on the top right corner of the profile in NI
2. Multisim webpage.

3. The schematic representation opens in a new tab.
4. Place three 'Ground' Schematic connector on the screen.
5. Place the logic gates from the digital section on the board, as per the
6. required circuit diagram for 4-bit Binary to BCD Converter
1. Now, add clock voltages to the input of the logic gate and connect them
7. with the help of Ground present in 'Schematic Connectors'.
2. Change the frequency of clock voltages e.g V1(say=5kHz) and V2(say=3kHz)
8. etc.
3. Connect a resistor to the output of the logic gate and then, Ground it with
9. the help of Ground Schematic Connector.
4. Connect the components with connecting wires.
5. Add digital probes to both input and output connections.
6. Set the display to 'Transient' from Interactive and press the 'Start
10. Simulation' button.
11. Note the graph

PRECAUTIONS:

1. All ICs should be checked before starting the experiment.
2. All the connection should be tight.
3. Always connect ground first and then the supply.
4. Switch off the power supply after completion of the experiment.

RESULT:

4-Bit Binary to BCD Converter has been studied and its truth table is verified.

Circuits and Output waveform

4-Bit Binary to BCD Converter - 1 x

multisim.com/content/xmHR3iyABHHGstFX8DYwbT/4-bit-binary-to-bcd-converter/


Apps Gmail YouTube Maps WhatsApp Member Portal | Int... (6) LinkedIn 200+ Attractive Ca... AES encryption Online Compiler an... Free Vectors, Photo... How To Create a BL...

MultisimLive FEATURES PRICING CIRCUITS RESOURCES HELLO, REEHA CREATE CIRCUIT

4-Bit Binary to BCD Converter

Favorite 0 Copy 0 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

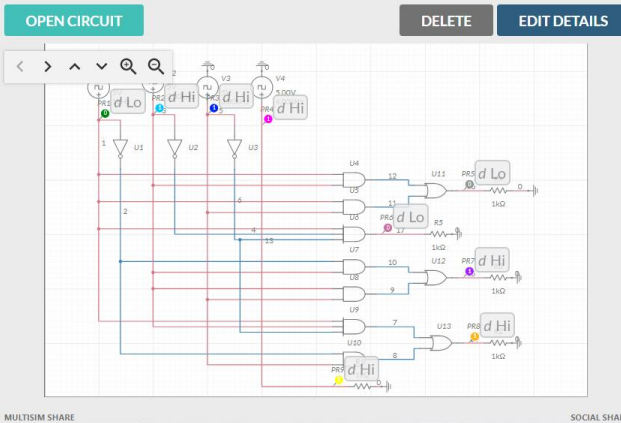

CREATOR reeha 29 Circuits

DATE CREATED 10 minutes ago LAST MODIFIED 0 minutes ago

TAGS This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

Online simulator by ElectroInferno 144171 22 522

Windows Taskbar: Type here to search, 12:25 02-12-2020

4-Bit Binary to BCD Converter - 1 x


multisim.com/content/xmHR3iyABHHGstFX8DYwbT/4-bit-binary-to-bcd-converter/

Apps Gmail YouTube Maps WhatsApp Member Portal | Int... (6) LinkedIn 200+ Attractive Ca... AES encryption Online Compiler an... Free Vectors, Photo... How To Create a BL...

MultisimLive FEATURES PRICING CIRCUITS RESOURCES HELLO, REEHA CREATE CIRCUIT

Circuit Graph

Interactive 1

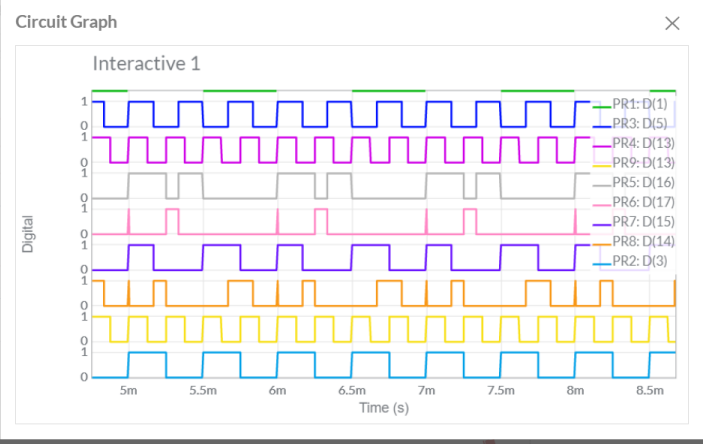

Digital

Time (s)

PR1: D(1)
PR3: D(5)
PR4: D(13)
PR9: D(13)
PR5: D(16)
PR6: D(17)
PR7: D(15)
PR8: D(14)
PR2: D(3)

CIRCUIT DESCRIPTION

No description has been provided for this circuit. EDIT DESCRIPTION

Digital to Analog Converter - DAC by SiLRing

Windows Taskbar: Type here to search, 12:26 02-12-2020

VIVA-VOCE QUESTIONS:

Q1. $(10110)_2 = (\quad ? \quad)_{BCD}$

Ans.

$(10110)_2 = (\quad \quad \quad)_{BCD}$

Q2. Convert decimal to BCD $(22)_{10} = (\quad \quad \quad)_{BCD}$

2	2
<u>0010</u>	<u>0010</u>

$\therefore (22)_{10} = (00100010)_{BCD}$

$\therefore (10110)_2 = (00100010)_{BCD}$

Q3. Write the algorithm to convert binary to BCD.

Ans.

Algorithm:

1. If any column (100's, 10's, 1's, etc.) is 5 or greater, add 3 to that column.
2. Shift all #'s to the left 1 position.
3. If 8 shifts have been performed, it's done! Evaluate each column for the BCD values.
4. Go to step 1.

100's	10's	1's	Binary	Operation
			1010 0010	← 162
		1	010 0010	<< #1
		10	10 0010	<< #2
		101	0 0010	<< #3
		1000		add 3
	1	0000	0010	<< #4
	10	0000	010	<< #5
	100	0000	10	<< #6
	1000	0001	0	<< #7
	1011			add 3
1	0110	0010		<< #8

↑ 1
 ↑ 6
 ↑ 2

Q4. Why do we convert Binary to BCD?

Ans.

Conversion of a binary number into separate binary numbers representing digits of the decimal number.

(this example is for 8-bits, other sizes follow the same pattern)

```
for(i=0; i<8; i++) {  
    //check all columns for >= 5  
    for each column {  
        if (column >= 5)  
            column += 3;  
  
        //shift all binary digits left 1  
        Hundreds <<= 1;  
        Hundreds[0] = Tens[3];  
        Tens <<= 1;  
        Tens[0] = Ones[3];  
        Ones <<= 1;  
        Ones[0] = Binary[7];  
        Binary <<= 1;  
    }  
}
```