

EXPERIMENT - 1

AIM: Realize all gates by verifying their truth tables.

HARDWARE REQUIRED: Power supply/ Voltage supply, Bread Board, Resistors, LEDs, Connecting Wires, Integrated Chips ICs (7404, 7408, 7432, 7486, 7400, 7402, 74266)

SOFTWARE REQUIRED:


Software stimulator (MULTISIM) - www.multisim.com (free software)

Stimulating schematic models of desired circuits


Components used - Source (Clock Voltage), Passive elements (resistor), Digital components (AND, OR, NAND, NOR, XOR, XNOR, Inverter), Probe for Analysis and annotation (Digital), Schematic connectors (Ground)

CIRCUIT:


AND GATE

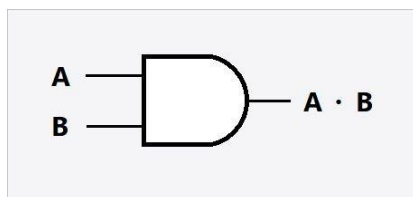


OR GATE

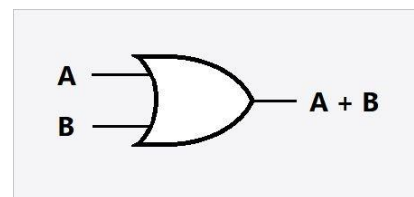


NAND GATE


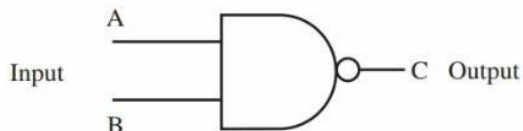


NOR GATE

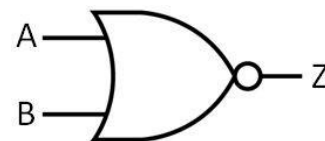


NOT GATE

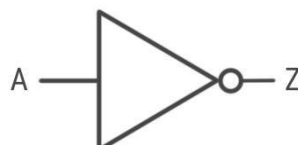

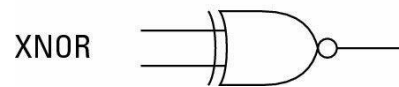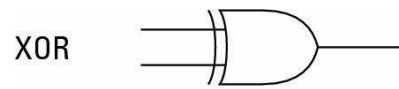


PIN - DIAGRAM:


AND GATE

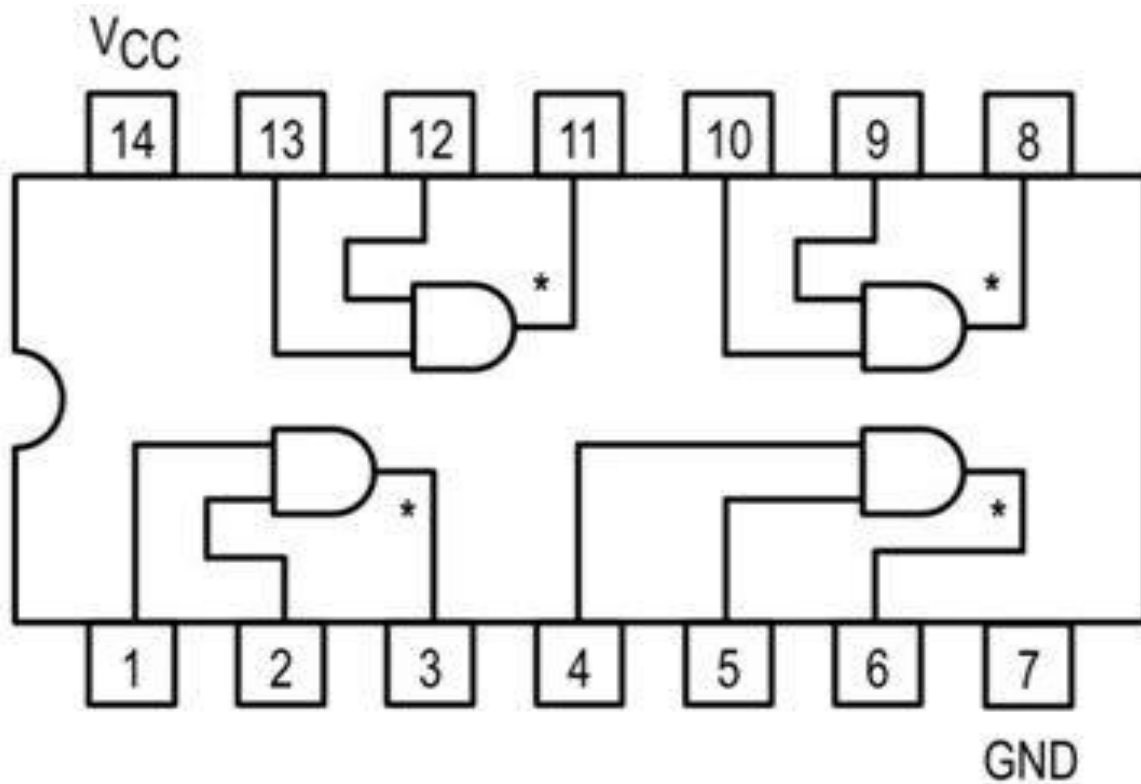


NAND GATE

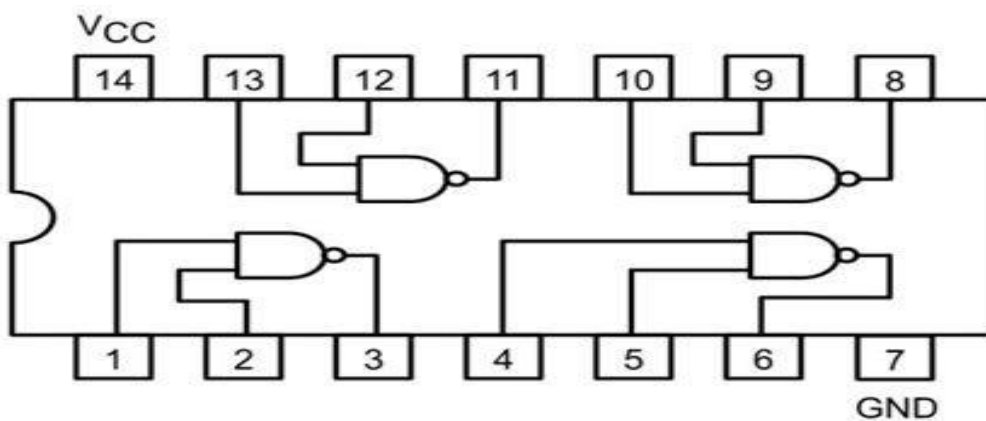


OR GATE

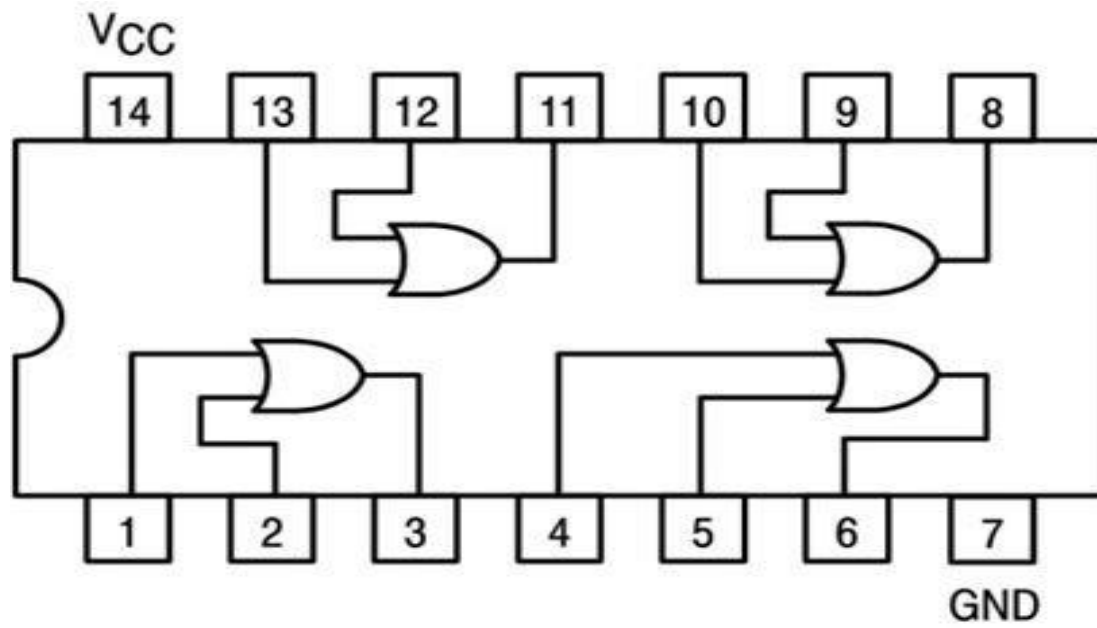


NOR GATE

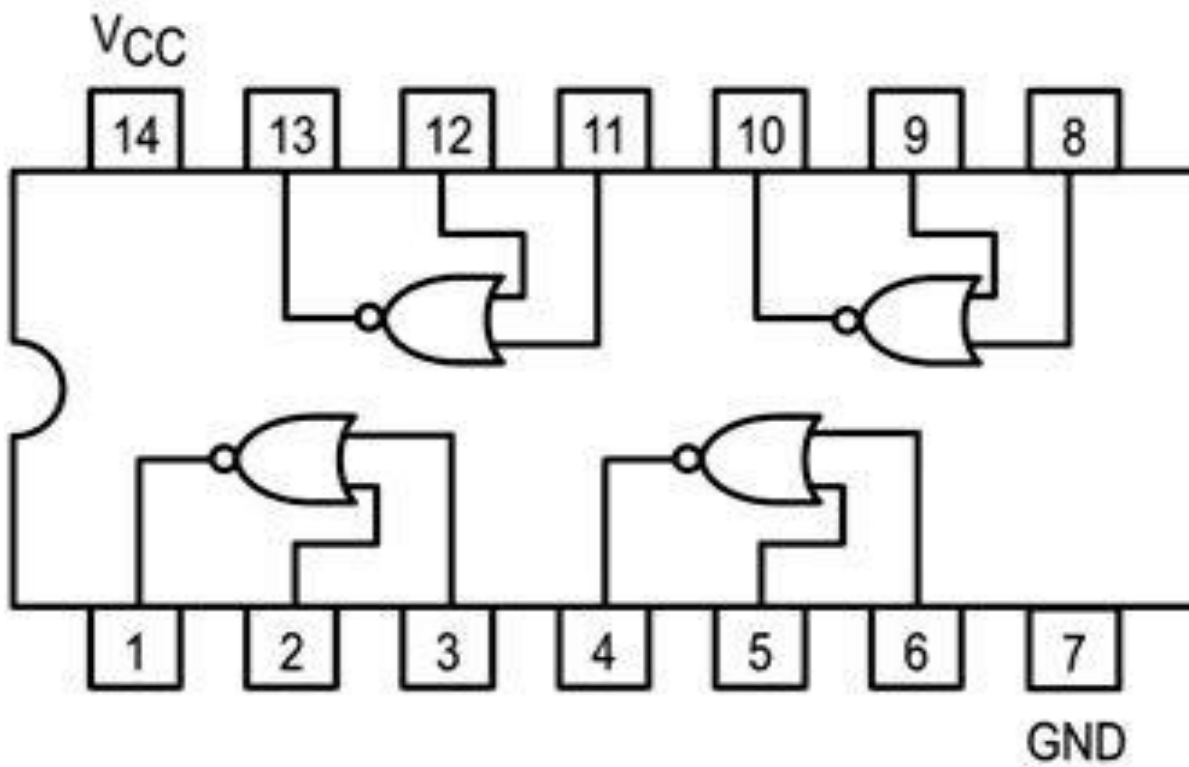


XOR GATE

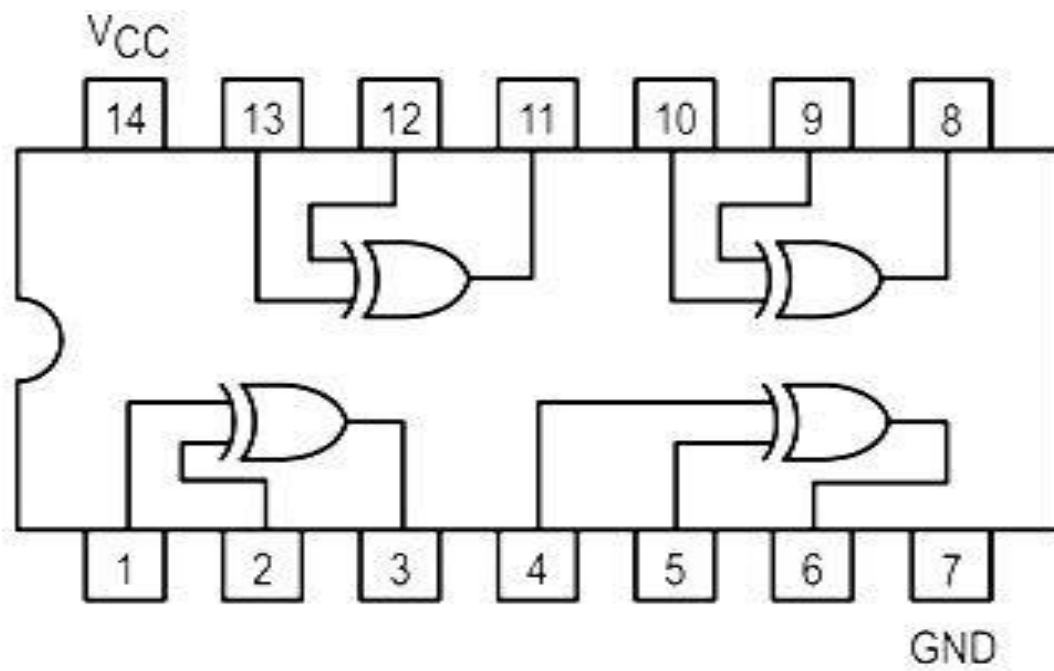

XNOR GATE

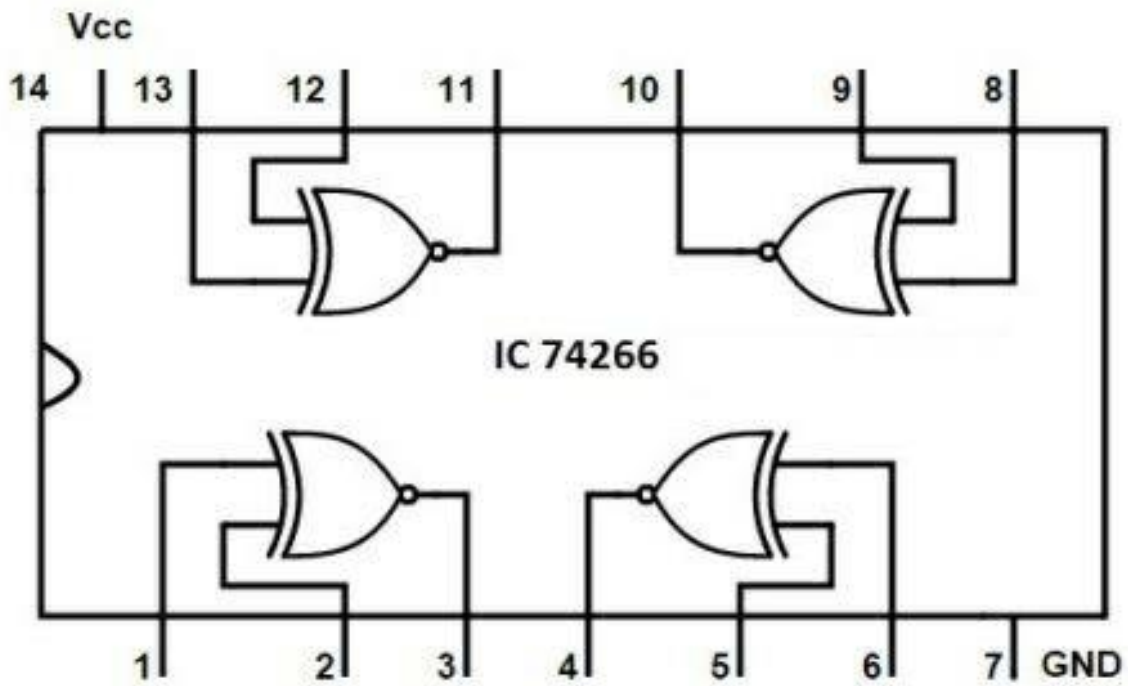

NOT GATE

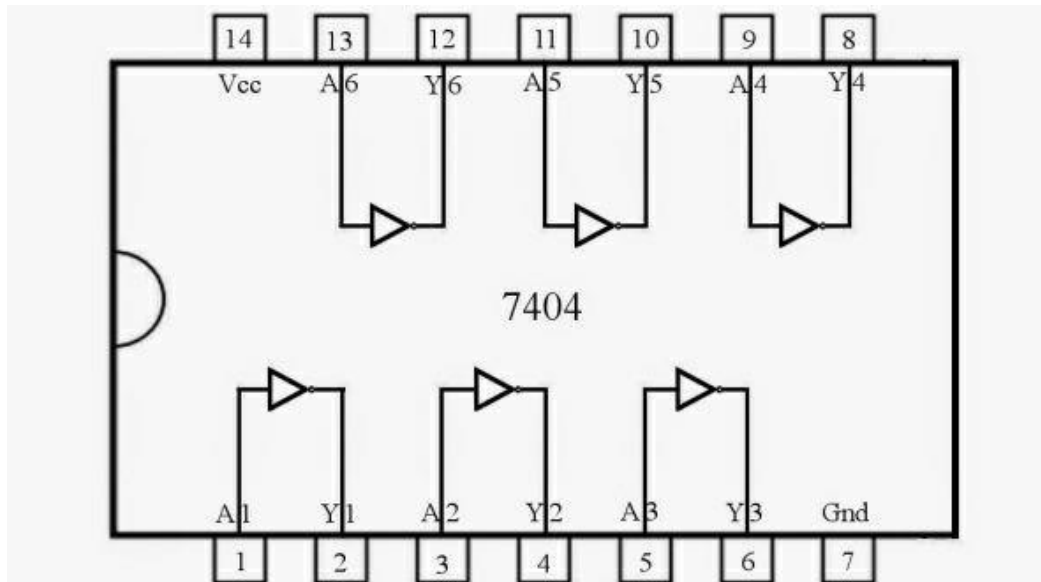

TRUTH TABLES

AND Truth Table		
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

NAND Truth Table		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

NOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

NOT Truth Table	
A	Q
0	1
1	0

XOR Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Or Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

THEORY: Logic gates are electronic circuits which perform logical operations on one or more inputs to produce a signal output. There are 7 logic gates. These include the AND, NAND, OR, NOR, XOR, XNOR and NOT.

PROCEDURE (MULTISIM):

- Make the circuits shown as shown in the figures.
- Select the required components (gates, resistor, voltage sources (Clock Voltage) and ground symbols from the tool bar on the left.
- Ground both the voltage sources (clock Voltages) and then connect them to the input terminal of the gate.
- Connect the output terminal to 1 k ohm resistor and ground it.

Precautions:

- Power supply should not exceed 5V.
- All the connections should be tight.
- Components should be tested before the practical.

NOT GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OPEN CIRCUIT DELETE EDIT DETAILS

< > ^ v Q

MULTISIM SHARE

CIRCUIT DESCRIPTION

CREATOR: reeha 7 Circuits

DATE CREATED: 0 minutes ago

LAST MODIFIED: 0 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno 99606 stars 11 339
- Simple Buck Converter by OStep 35348 stars 22 268

Circuit Graph

Interactive 1

Time (s)

Digital

PR1: D(2)

PR2: D(1)

No description has been provided for this circuit. EDIT DESCRIPTION

Digital to Analog Converter - DAC by SILRing 24061 stars 31 98

13:33 26-08-2020

XNOR GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

XNOR Gate

★ Favorite 0 Copy 0 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha (7 Circuits)


DATE CREATED: 2 minutes ago LAST MODIFIED: 2 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by Electronferno (99606 views, 11 stars, 339 likes)
- Simple Buck Converter by OStep

Waiting for faye.getstream.io...

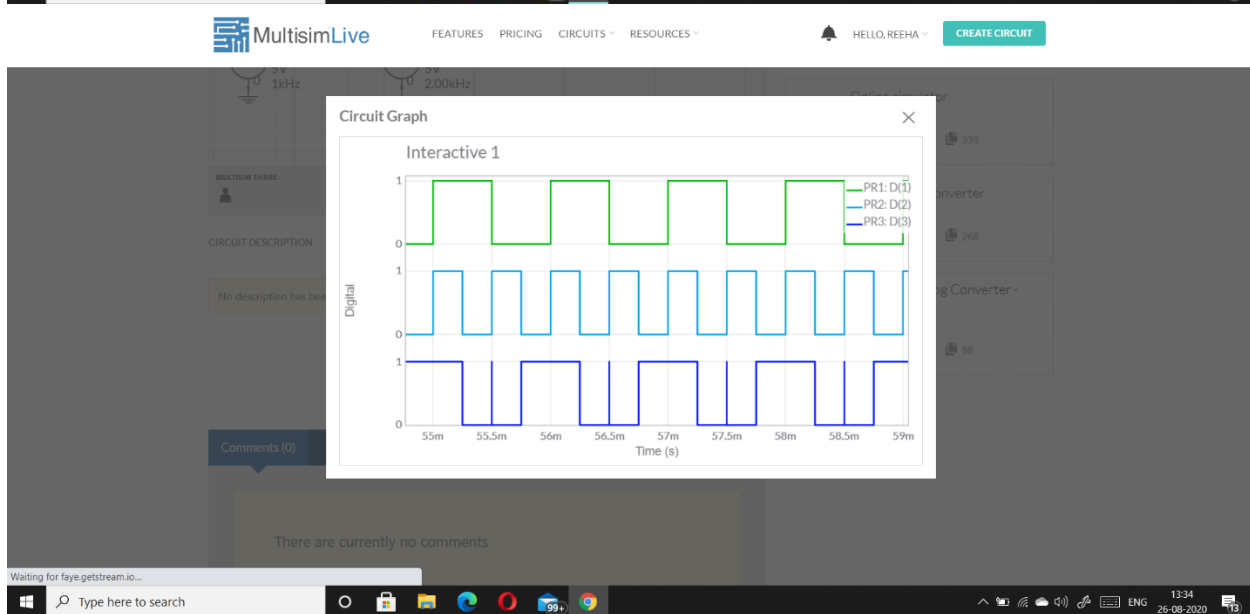

XOR GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 7 Circuits

DATE CREATED: 5 minutes ago LAST MODIFIED: 5 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by Electronforno 99606 stars 11 339
- Simple Buck Converter by OStep 35348 stars 22 268

CIRCUIT DESCRIPTION

Waiting for faye.getstream.io...

Type here to search

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 7 Circuits

DATE CREATED: 5 minutes ago LAST MODIFIED: 5 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by Electronforno 99606 stars 11 339
- Simple Buck Converter by OStep 35348 stars 22 268

CIRCUIT DESCRIPTION

No description has been provided for this circuit. EDIT DESCRIPTION

Waiting for faye.getstream.io...

Type here to search

NOR GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

NOR Gate

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha, 7 Circuits

DATE CREATED: 15 minutes ago LAST MODIFIED: 8 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno (99606 views, 11 stars, 339 likes)
- Simple Buck Converter by OStep (35348 views, 22 stars, 268 likes)

CIRCUIT DESCRIPTION

Windows taskbar: Type here to search, 13:34, 26-08-2020

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

NOR Gate

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha, 7 Circuits

DATE CREATED: 15 minutes ago LAST MODIFIED: 8 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno (99606 views, 11 stars, 339 likes)
- Simple Buck Converter by OStep (35348 views, 22 stars, 268 likes)

CIRCUIT DESCRIPTION

No description has been added for this circuit.

Circuit Graph

Interactive 1

Windows taskbar: Type here to search, 13:35, 26-08-2020

OR GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OR Gate

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 7 Circuits

DATE CREATED: 11 minutes ago

LAST MODIFIED: 11 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

CIRCUIT COPIED FROM: NOR Gate

MOST POPULAR CIRCUITS

- Online simulator by Electronforno (99606 views, 11 likes, 339 shares)
- Simple Buck Converter

MULTISIM SHARE

CIRCUIT DESCRIPTION

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

Circuit Graph

Interactive 1

PR1: D(1)
PR2: D(2)
PR3: D(3)

Time (s)

Comments (0)

There are currently no comments

NAND GATE

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

NAND Gate

OPEN CIRCUIT

DELETE

EDIT DETAILS

PR1 d Hi

PR2 d Hi

PR3 d Lo

V1 5V 1kHz

V2 5V 1.50kHz

U1

R1 1kΩ

0

CREATOR

reeha

7 Circuits

DATE CREATED

14 minutes ago

LAST MODIFIED

14 minutes ago

TAGS

This circuit has no tags currently.

EDIT TAGS

MOST POPULAR CIRCUITS

Online simulator by ElectroInferno

99606 11 339

Simple Buck Converter by Ostep

268 38

MULTISIM SHARE

SOCIAL SHARE

Type here to search

1336 26-08-2020

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA

CREATE CIRCUIT

Circuit Graph

Interactive 1

PR1: D(1)

PR2: D(2)

PR3: D(3)

Digital

Time (s)

Comments (0)

There are currently no comments

Type here to search

1336 26-08-2020


AND GATE

OPEN CIRCUIT

DELETE

EDIT DETAILS

< > ^ v 🔍

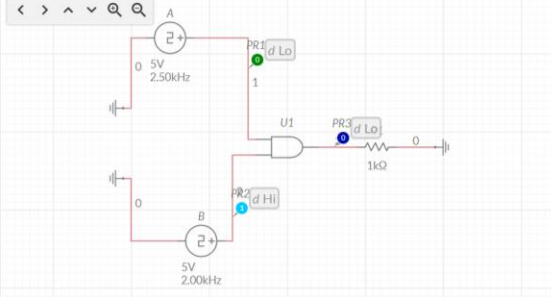

MULTISIM SHARE

</> 🔗 📧 🌐 📱

SOCIAL SHARE

👤

CIRCUIT DESCRIPTION

Waiting for faye.getstream.io...

CREATOR

reeha

7 Circuits

DATE CREATED

33 minutes ago

LAST MODIFIED

27 minutes ago

TAGS

This circuit has no tags currently.

EDIT TAGS

MOST POPULAR CIRCUITS

Online simulator

by ElectronInferno

99606 ★ 11 339

Simple Buck Converter

by OStep

35348 ★ 22 268

Waiting for faye.getstream.io...

Type here to search

🏠 📁 🌐 🔄 📶 📱

13:36 26-08-2020

MULTISIM SHARE

CIRCUIT DESCRIPTION


No description has been added.

Comments (0)

There are currently no comments

Circuit Graph

Interactive 1

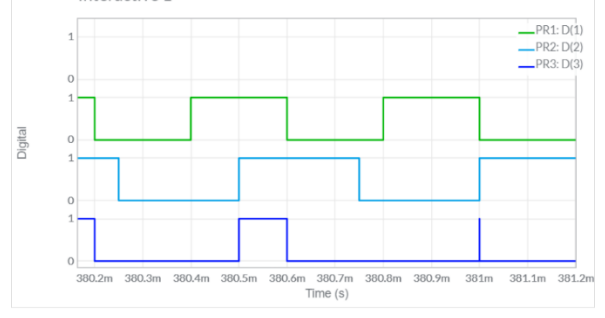

Waiting for faye.getstream.io...

Type here to search

🏠 📁 🌐 🔄 📶 📱

13:36 26-08-2020