



EXPERIMENT 2

Switching Theory and Logic Design (STLD)

Aim

To verify the truth tables of all logical gates(AND, OR, NOT, NAND, NOR, XOR, XNOR) **using NAND gate** only.

Syeda Reeha Quasar

14114802719

3C7

EXPERIMENT 2

Aim:

To verify the truth tables of all logical gates (AND, OR, NOT, NAND, NOR, XOR, XNOR) using NAND gate.


Hardware and Software Apparatus Required

Hardware: Power supply, Bread Board, Connecting Wires, respective IC, LED, Wire Cutter.

- ❖ Circuit is designed on bread board using Integrated Chips (ICs), Voltage supply and LEDS.
- ❖ The set-up of apparatus and working of the circuit were demonstrated via recorded videos.

Software Simulation: The schematic models of the desired circuits will be stimulated on MULTISIM (Free Software), easily accessible at www.multisim.com: Sign Up and create a profile.

Circuit (SYMBOL)

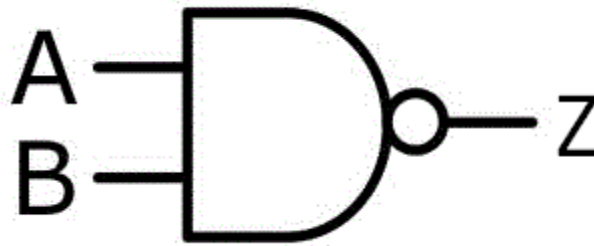


Digital Logic NAND Gate – Universal Gate

$$\text{Output} = \overline{A.B}$$

IC pin diagram

NAND GATE (IC 7400)

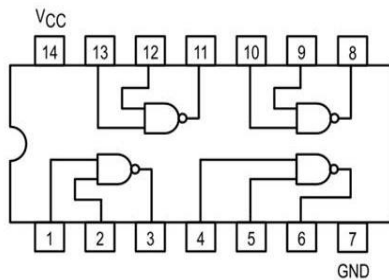

Truth Table

NAND GATE

NAND Truth Table		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Relevant Theory

NAND Gate

- The Boolean expression for a logic NAND gate is denoted by a single dot or full stop symbol, (.) with a line or Overline, ($\overline{}$) over the expression to signify the NOT or logical negation of the NAND gate giving us the Boolean expression of: $A.B = Q$.
- It is a series of AND gate followed by NOT gate. If the output is 0 then any or all inputs are 1. Otherwise, output is 1.
- **It is a universal gate:** Universal Logic gates can be used to produce any other logic or Boolean function with the NAND and NOR gates being minimal. Individual logic gates can be connected together to form a variety of different switching functions and combinational logic circuits.

Procedure followed on MULTISIM

1. LOG IN ON www.multisim.com
2. CREATE THE CIRCUIT
3. SAVE THE CIRCUIT

4. SAVE THE SCREENSHOTS FOR
 - i. INPUT & OUTPUT WAVEFORMS (ALONG WITH YOUR ID ON TOP LEFT)
 - ii. CIRCUIT (ALONG WITH YOUR ID ON TOP LEFT)

Screenshot of Circuit: *NOT(INVERTER) USING NAND*

multisim.com/content/JZw8HUqvyCA6h6vDdvrASR/not-from-nand/

Apps Gmail YouTube Maps WhatsApp Member Portal | Int... (6) LinkedIn 200+ Attractive Ca... AES encryption Online Compiler an... Free Vectors, Photo... How To Create a BL...

MultisimLive FEATURES PRICING CIRCUITS RESOURCES HELLO, REEHA CREATE CIRCUIT

NOT from NAND

★ Favorite 0 Copy 0 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

< > ^ v Q Q

PR1 d Lb V2 5V 1kHz 0

U1

PR2 d Hi 1kΩ 0

MULTISIM SHARE SOCIAL SHARE

CREATOR reeha 13 Circuits

DATE CREATED 1 hour, 13 minutes ago LAST MODIFIED 0 minutes ago

TAGS This circuit has no tags currently. EDIT TAGS


MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno 101653 stars 11 349
- Simple Buck Converter by OStep

Type here to search

13:42 02-09-2020 ENG

Input waveform and Output waveform

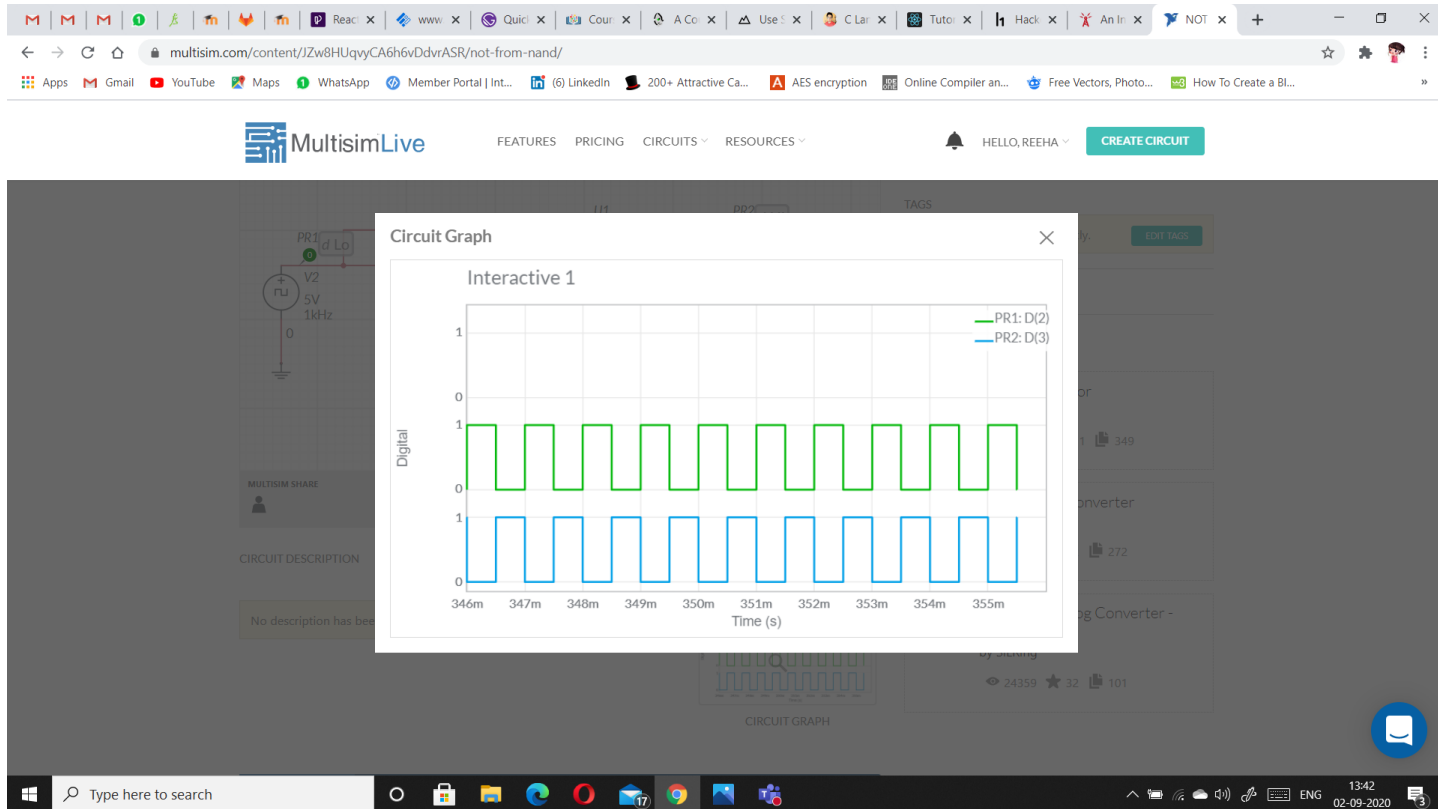

Screenshot of Circuit: *AND USING NAND*

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

AND from NAND

Favorite 0 Copy 0 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

CREATOR: reeha 13 Circuits

DATE CREATED: 1 hour, 6 minutes ago LAST MODIFIED: 1 hour, 6 minutes ago

TAGS: This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS

- Online simulator by ElectroInferno 101653 stars 11 349
- Simple Buck Converter by OStep 101

MULTISIM SHARE SOCIAL SHARE

Input waveform and Output waveform

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

Circuit Graph

Interactive 1

PR1: D(2)
PR2: D(1)
PR3: D(4)

Digital

Time (s)

Comments (0)

There are currently no comments

MultisimLive

FEATURES PRICING CIRCUITS RESOURCES

HELLO, REEHA CREATE CIRCUIT

OR from NAND

★ Favorite 0 📄 Copy 0 👁 Views 1

OPEN CIRCUIT DELETE EDIT DETAILS

V1 5V 1kHz
V2 0.5V 1.50kHz
R1 1kΩ

CREATOR reeha 13 Circuits


DATE CREATED 23 minutes ago LAST MODIFIED 23 minutes ago

TAGS This circuit has no tags currently. EDIT TAGS

MOST POPULAR CIRCUITS


- Online simulator by ElectroInferno
👁 101654 ★ 11 📄 349
- Simple Buck Converter by OStep

Input waveform and Output waveform

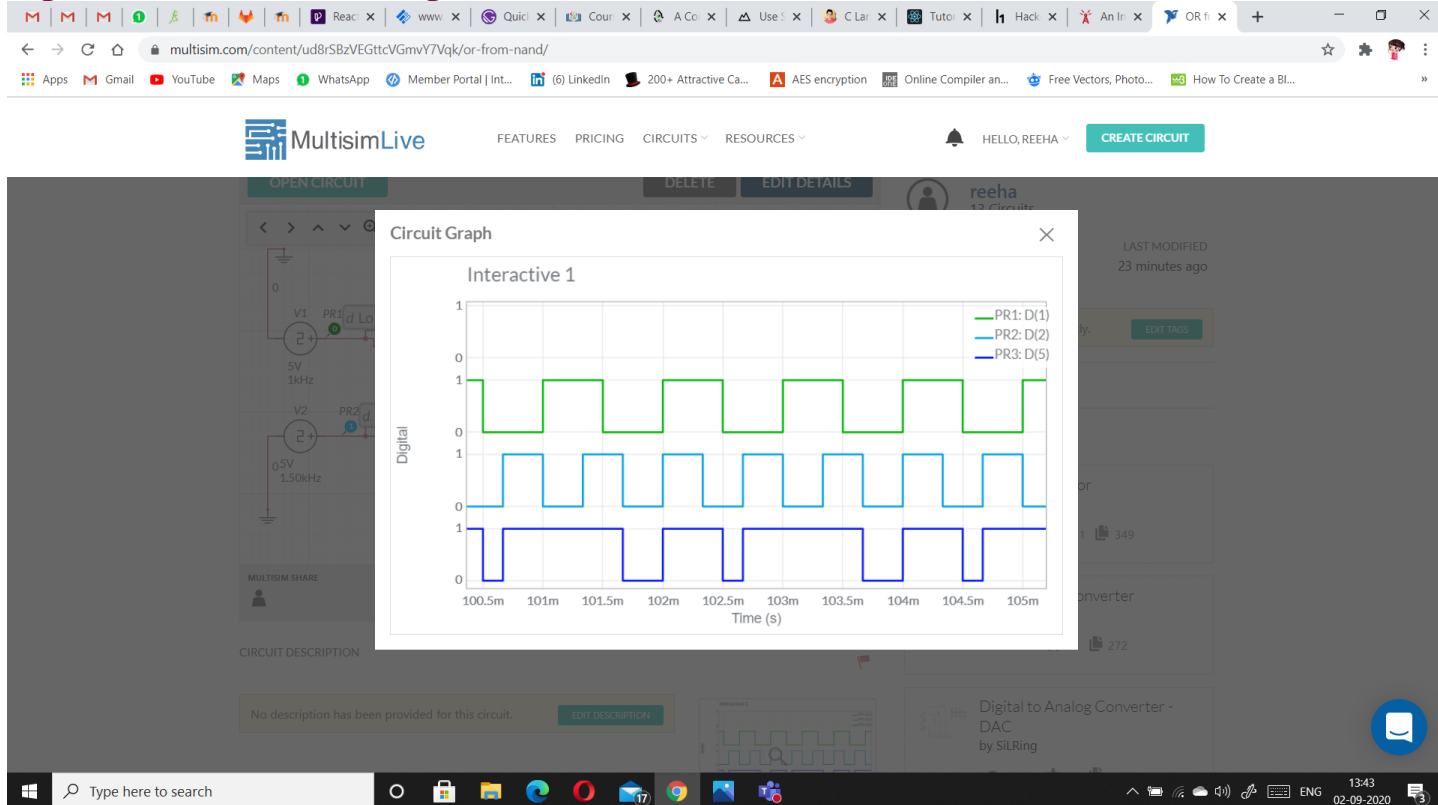

[illegible]

Input waveform and Output waveform

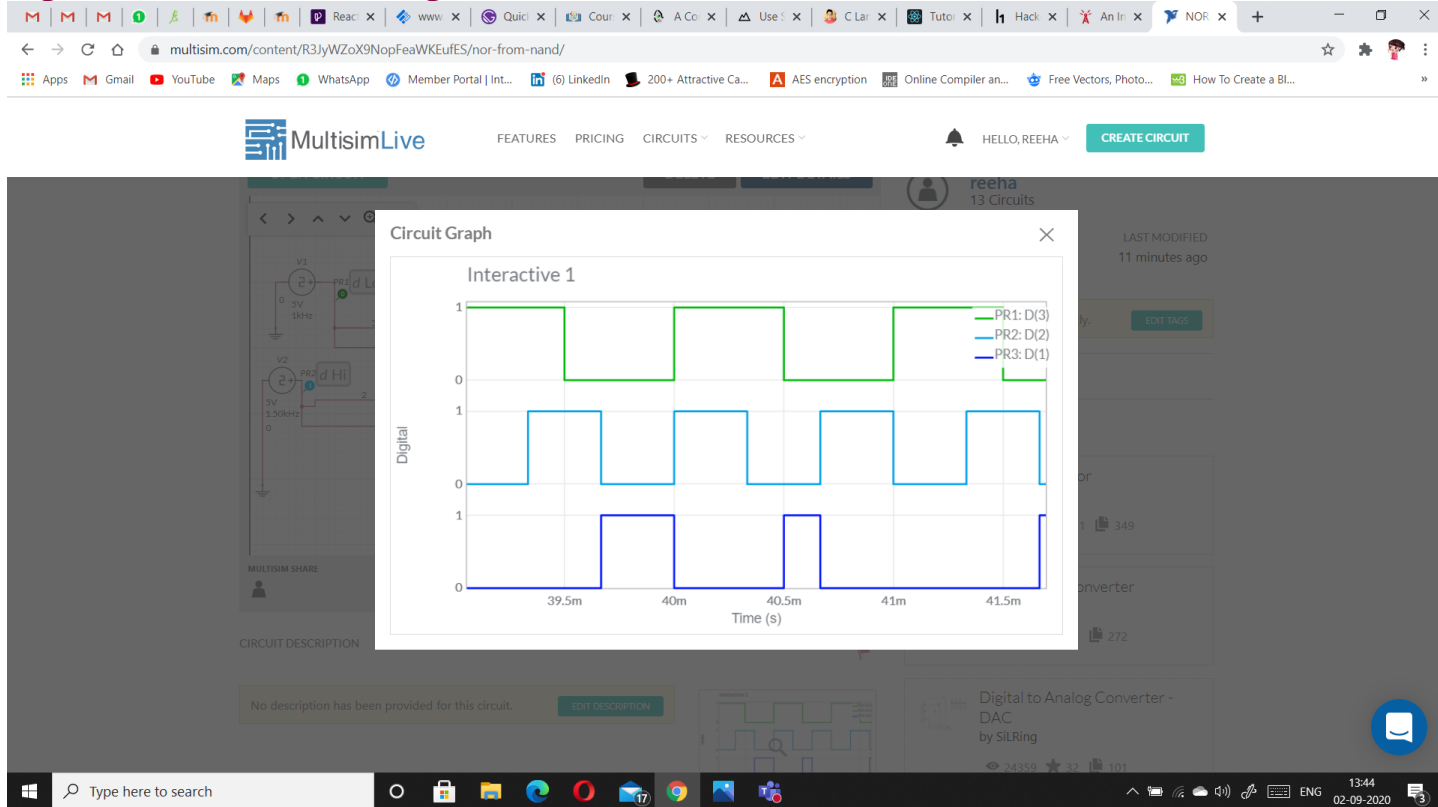


Screenshot of Circuit: *XOR USING NAND*

OPEN CIRCUIT

DELETE

EDIT DETAILS

< > ^ v 🔍

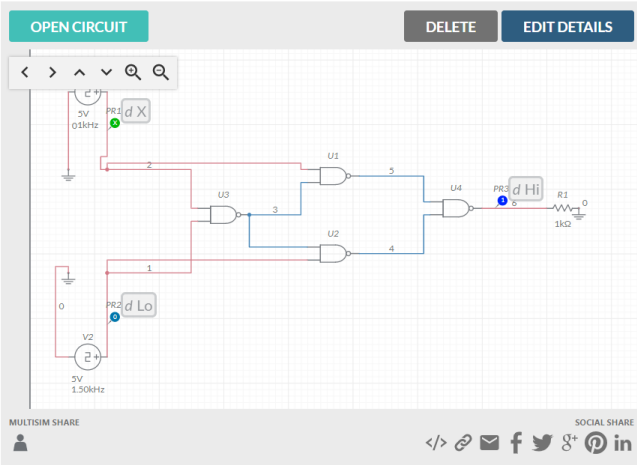

MULTISIM SHARE

SOCIAL SHARE

CREATOR

reeha

13 Circuits

DATE CREATED

17 minutes ago

LAST MODIFIED

16 minutes ago

TAGS

This circuit has no tags currently.

EDIT TAGS

MOST POPULAR CIRCUITS

Online simulator

by ElectroInferno

101655 11 349

Simple Buck Converter

by OStep

35790 22 272

CIRCUIT DESCRIPTION

Windows Taskbar

13:44 02-09-2020

[illegible]

M M M React x www x Quic x A Co x Use x C Lar x Tutor x Hack x An In x XNO x +

< > ↺ 🏠 multisim.com/content/KYmozfZPWfHFDLyaCUScZG/xnor-fron-nand/ ☆ ⚙️ 👤 :

Apps Gmail YouTube Maps WhatsApp Member Portal | Int... (6) LinkedIn 200+ Attractive Ca... AES encryption Online Compiler an... Free Vectors, Photo... How To Create a BL...

MultisimLive

FEATURES PRICING CIRCUITS ▾ RESOURCES ▾

HELLO, REEHA ▾

[CREATE CIRCUIT](#)

XNOR from NAND

★ Favorite 0 📄 Copy 0 👁 Views 1

OPEN CIRCUIT

DELETE EDIT DETAILS

< > ^ v 🔍

MULTISIM SHARE SOCIAL SHARE

CREATOR

reeha
13 Circuits

DATE CREATED
6 minutes ago
 LAST MODIFIED
6 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)


MOST POPULAR CIRCUITS

Online simulator
by Electroliferno

👁 101655 ★ 11 📄 349

Simple Buck Converter
by Ostep

Input waveform and Output waveform

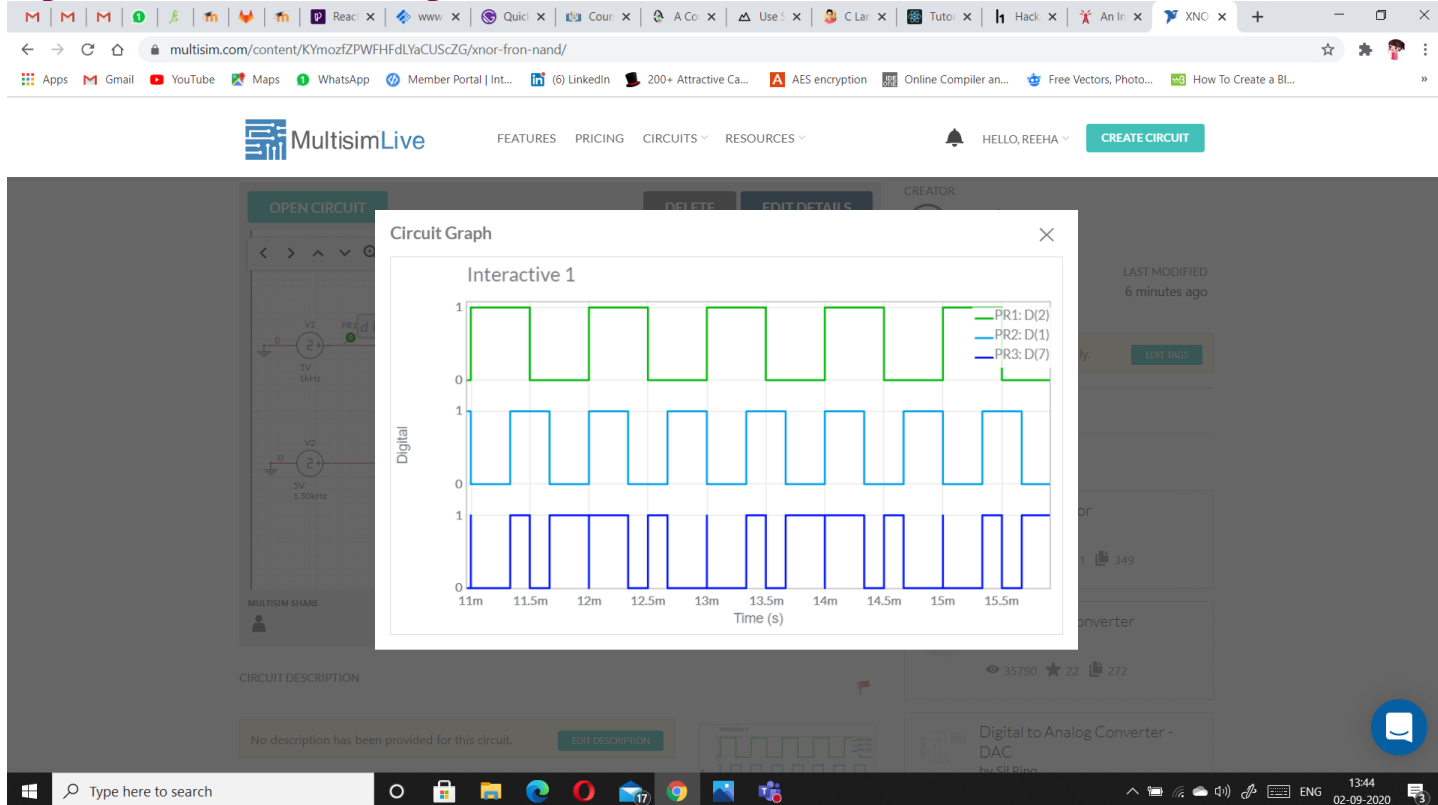

Precautions (MULTISIM):

1. Frequency of clock voltage source should be different for both inputs.
2. Place the probes carefully only at the input and output sources.
3. Use digital analyzer probe.
4. Set the type to transient.
5. Ground both the voltage sources(clock) and the resistor.